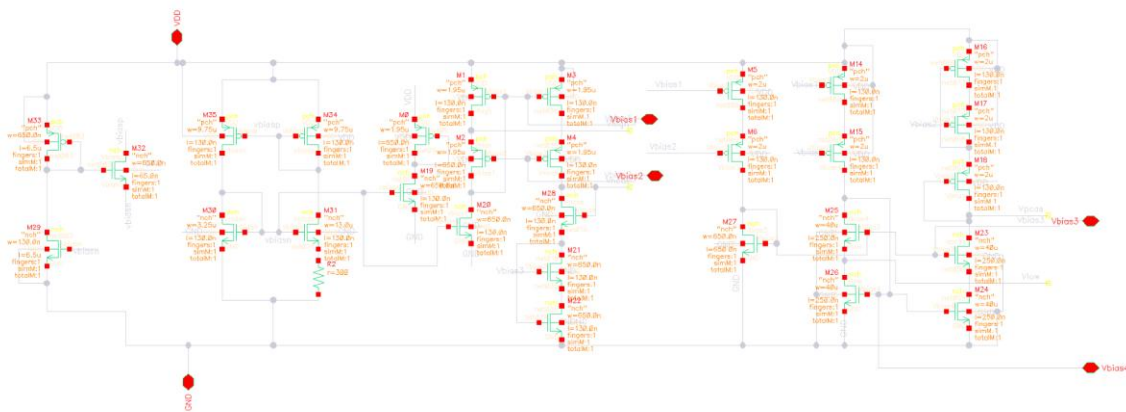


ELEG 587V Project #1 (100 pts)


For both parts, you are to utilize Cadence Virtuoso to design the necessary circuits. You supply voltage should be no larger than 1.2 V, and the circuits should be fully contained (i.e., you only provide the input signals and the power). You will write a short report and turn in all necessary schematics, simulations, and waveforms.

1.Design a Beta-Multiplier circuit that provides a reference current of between 100 μA to 500 μA . The Beta-Multiplier should feed into a general biasing circuit that provides four unique biasing levels. Turn in the schematic and DC simulation with the output bias voltages.

SCHEMATIC:




TESTBENCH:

 


SIMULATIONS:


ID vs VDD Curve:

 


VBIAS1= 404.4mV:

 


VBIAS2= 408.34 mV:

 

VBIAS3= 94.55 mV:

 


VBIAS4= 168 mV:

 


2. Design a differential amplifier (you can choose which topology) that provides a gain between 60-100 dB. Higher gains will receive more points. The differential amplifier should receive all its

biasing from Part #1's circuit. Provide simulations for a 50 mV sine input signal at 100 kHz, 1 MHz, 10 MHz, 100 MHz, 1 GHz, and 10 GHz. Find the input common-mode range in simulation and provide the Bode plot of the gain magnitude and phase of the amplifier.

SCHEMATIC:

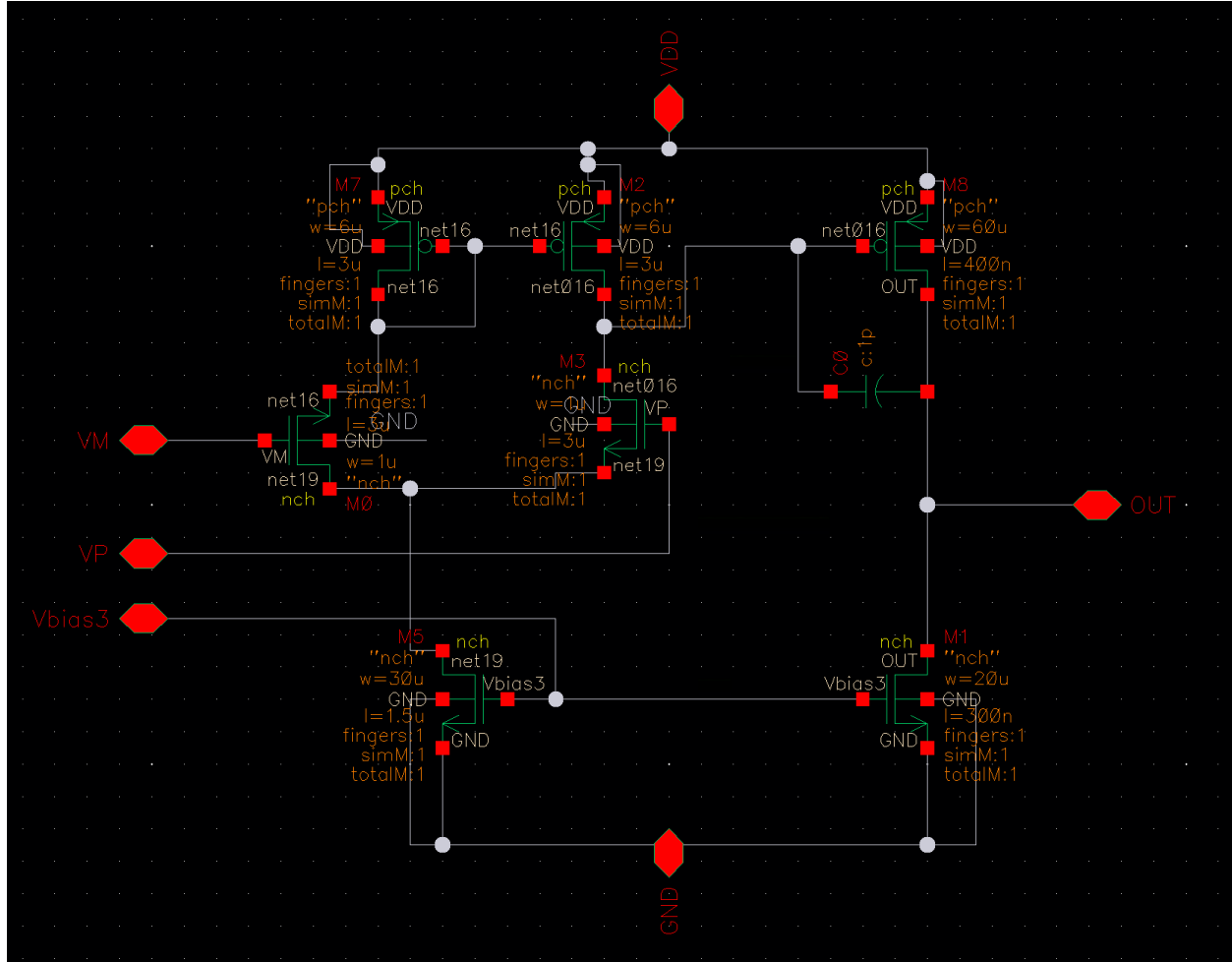

TESTBENCH:

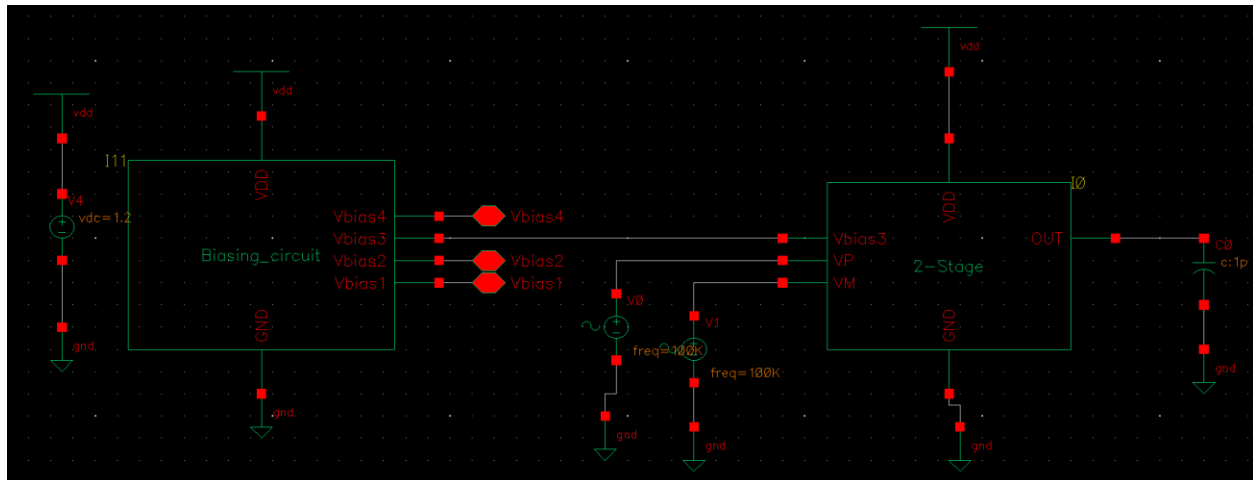


SIMULATIONS:


GAIN (dB):

DC Voltage $V_P = V_M = 600\text{mv}$


AC magnitude= 1.5V

 


Phase Margin:

 


50mv at 100Khz

 


50mv at 1M

 


50mv at 10Mhz

 


50mv at 100M

 

50mv at 1G

 


50mv at 10G

 

3. Provide a compact analog friendly layout that utilizes guard rings and common-centroid techniques for Parts #1 and #2.

Part #1 Layout

 

DRC check

Calibre - RVE v2011.4_35.27: Biasing_circuit_copy.drc.results

File View Highlight Tools Window Setup Help

Find:

Topcell Biasing_circuit_copy, 0 Results (in 0 of 3 Checks) Show All

Check / Cell

✓ Check DENSITY_PR


00.DN.2H_IO.density
00.DN.2H_CORE.density
00.DN.3L.density
00.DN.3H_IO.density
00.DN.3H_CORE.density
P0.DN.3.density
M1.DN.1.1.density
M1.DN.2.density
M1.DN.4.density
M2.DN.1.1.density
M2.DN.2.density
M2.DN.4.density
M3.DN.1.1.density
M3.DN.2.density

Check DENSITY_PRINT_FILES, 0 Cells: 0 Results

[illegible]

The schematic includes a capacitor as well, but for the final layout the capacitor is excluded from the checks as placing it resulted in VMware to hang/stop responding for greater periods of time, delaying our work.

Part #2 layout

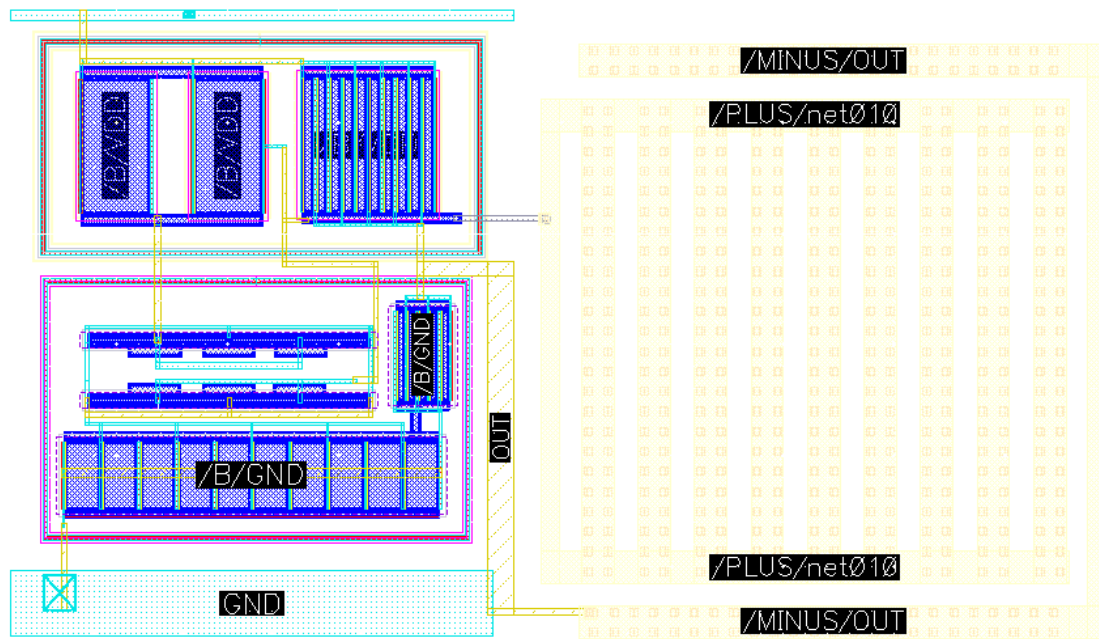

DRC check

Calibre - RVE v2011.4_35.27: 2_Stage_Project_Final_for_layout_copy.drc.results

File View Highlight Tools Window Setup Help

Find:

Topcell 2_Stage_Project_Final_for_layout_copy, 0 Results (in 0 of 3 Checks) Show All

Check / Cell

Check DENSITY_PR

00.DN.2H_IO.density
00.DN.2H_CORE.density
00.DN.3L.density
00.DN.3H_IO.density
00.DN.3H_CORE.density
P0.DN.3.density
M1.DN.1.1.density
M1.DN.2.density
M1.DN.4.density
M2.DN.1.1.density
M2.DN.2.density
M2.DN.4.density
M3.DN.1.1.density
M3.DN.2.density

Check DENSITY_PRINT_FILES, 0 Cells: 0 Results

Final Layout

