
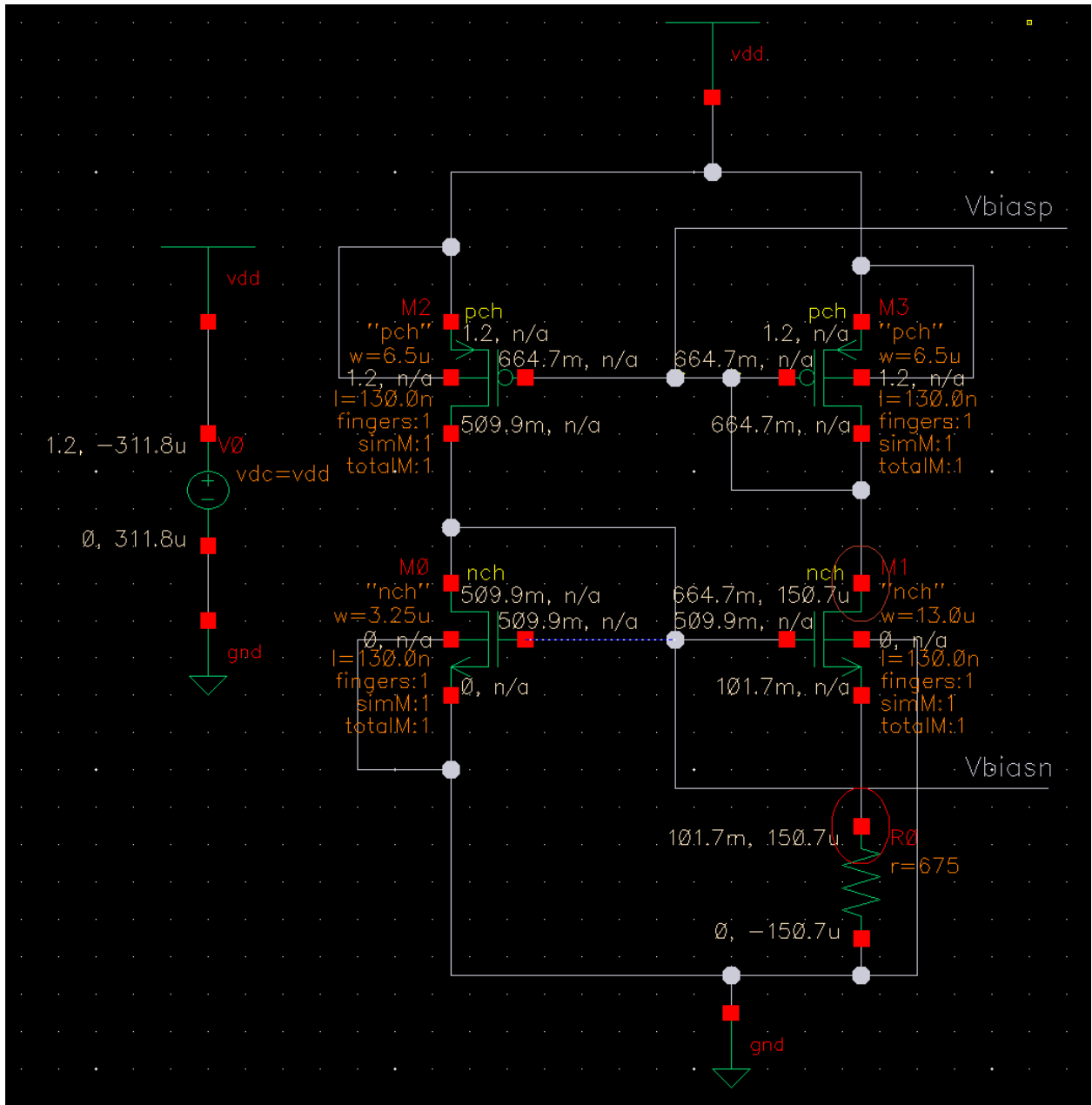


ELEG 587V Homework #1 (50 pts)

For all problems, you are to choose all the transistor properties that are required to meet the desired specification for the circuit as well as draw the circuit. Please box or underline all answers. Design both circuits within the MUSE 65nm technology within Cadence Virtuoso.

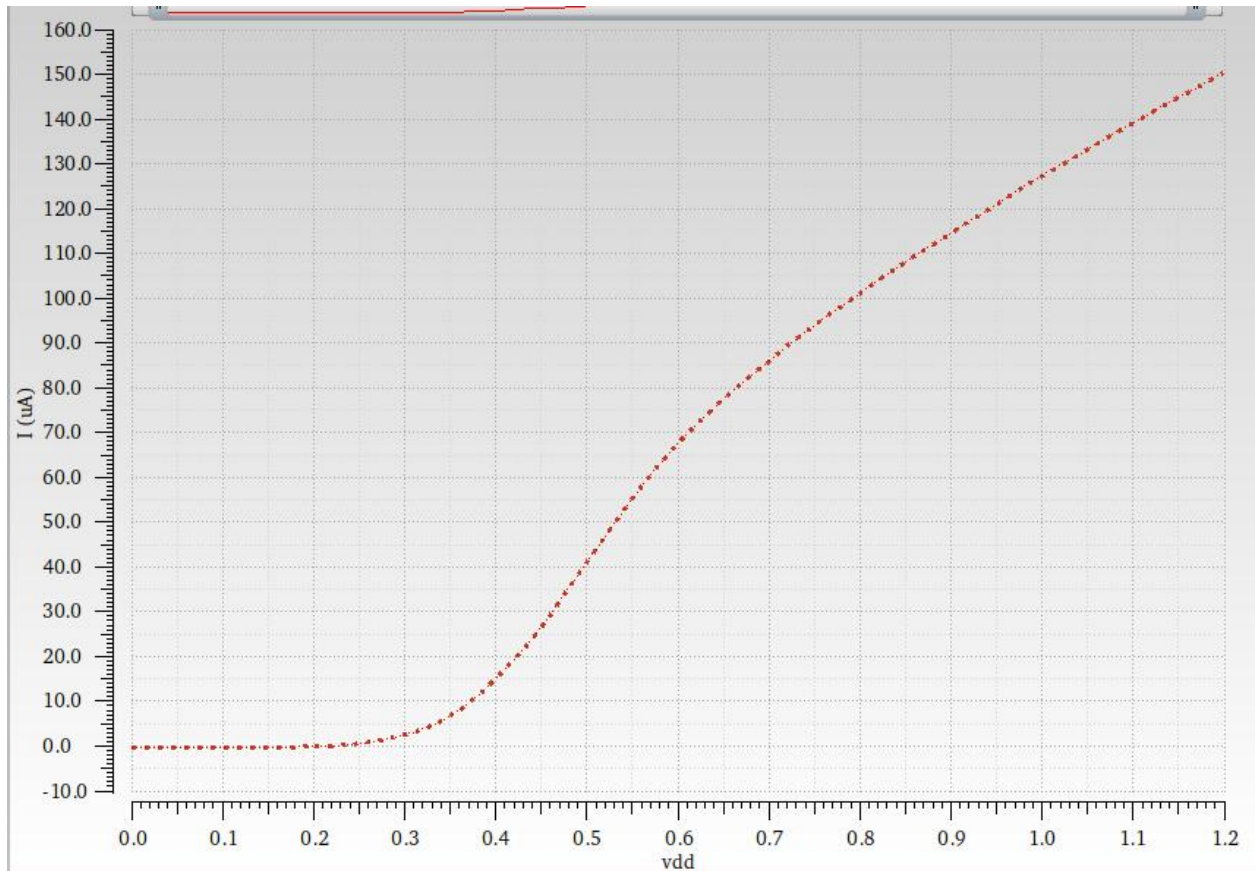- Design the simplest Beta-Multiplier circuit (no start-up circuit required) that provides a reference current of $150\ \mu\text{A}$. Give the resistance and the two bias voltages as your answers.







$R=675\Omega$

$V_{biasn}= 509.9\text{ mV}$

$V_{biasp}= 664.7\text{ mV}$

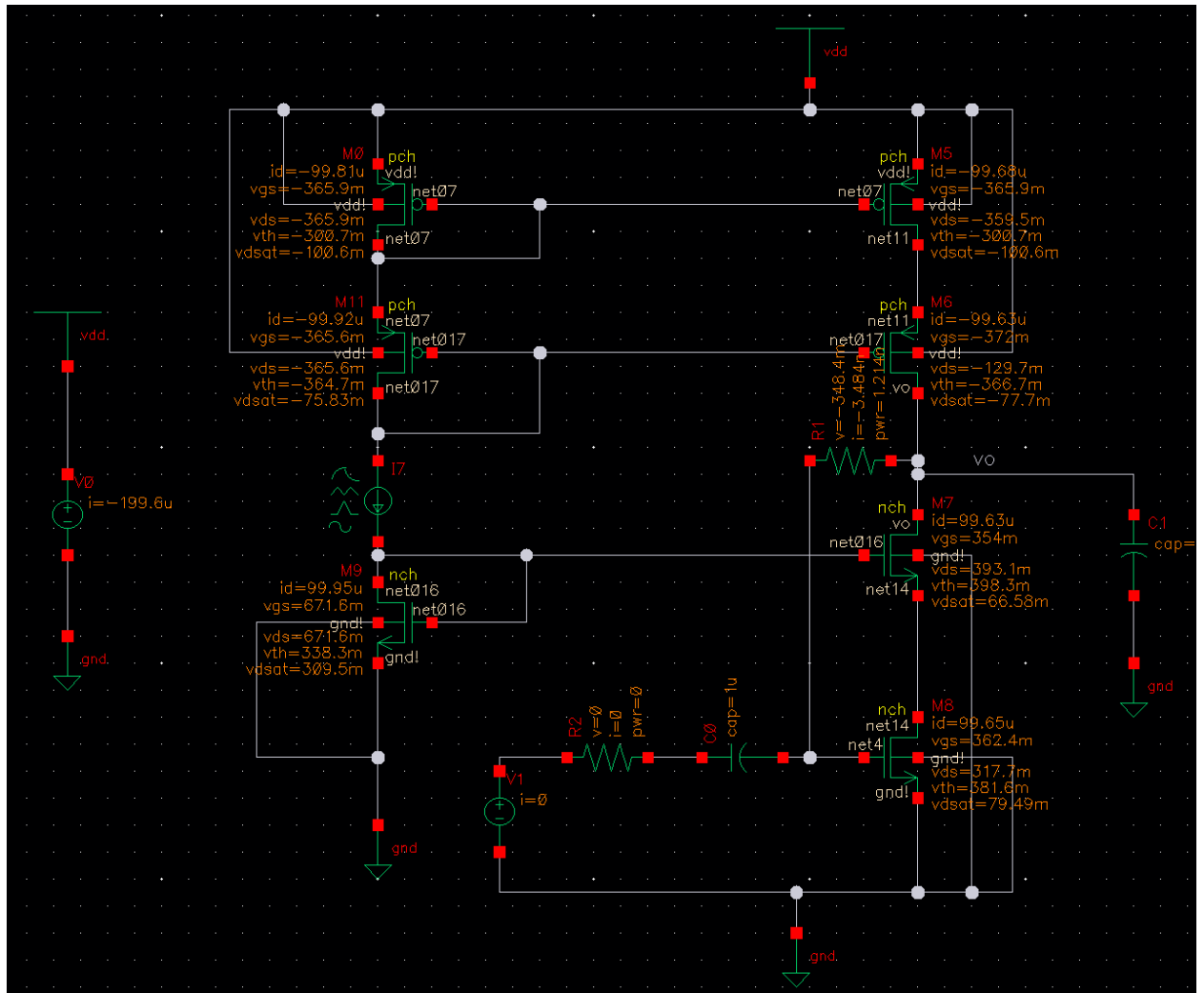- Design a common-source amplifier with a current source load that provides $100\text{ }\mu\text{A}$ to the amplifier with a voltage gain of 1000. Provide the input and output frequencies as well as the RHP zero frequency



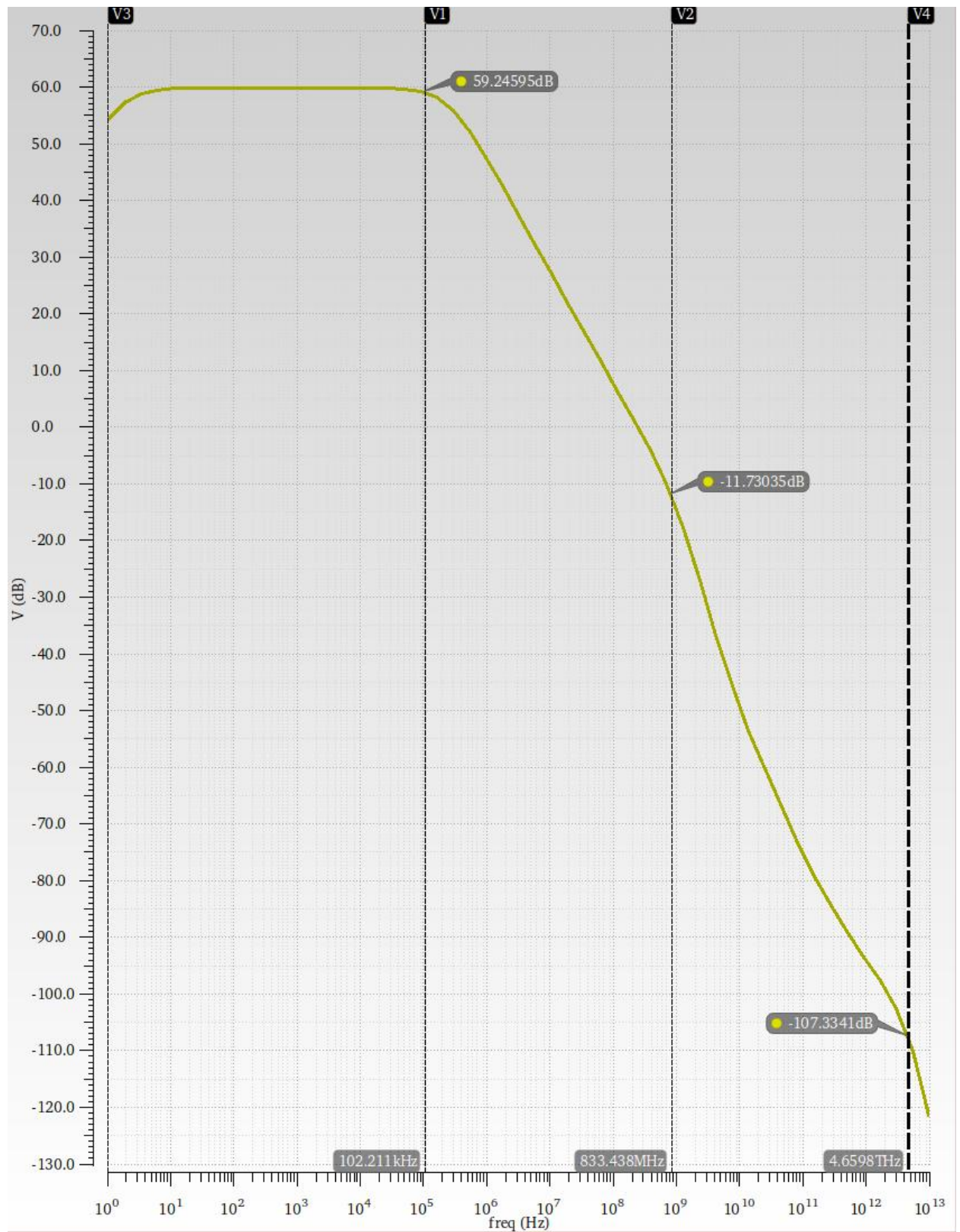

From the graph above it can be estimated that

Aireen Amir Jalal- 010989584

Analog IC Design

$F_{in}=f_{3db}=121\text{Khz}$

$F_{out}=880\text{Mhz}$

$F_z=4.5\text{Thz}$